




# 241 Notes (post-midterm)
 
## Finite State Machines (FSMs)



An FSM is a sequential circuit that has inputs  $w$ , outputs  $z$ , and flip-flops  $y$




The FSM has a state at any given clock cycle, which is represented by  $y_1, \dots, y_k$ . The next state  $Y_1, \dots, Y_K$  when a clock cycle occurs depends on the values of inputs  $w$ , and the present state  $y_1, \dots, y_k$
 
### Example: 3 States of Copper — happy, sad, and mad

Changes in state depend on  $w$  which represents Copper getting a treat.

- On a clock edge, if  $w = 1$ , copper is happy
  - Happy
- If Happy and  $w = 0$ , then
  - Sad
- If Sad and  $w = 0$ , then
  - Mad
- If Mad
  - Output  $z = 1$  (barking)



Present State	Next State		Output
	w=0	w=1	
Happy	Sad	Happy	0
Sad	Mad	Happy	0
Mad	Mad	Happy	1

In this example, we have used two flip flops (the minimum possible).

## General Procedure to Build an FSM

1. Draw the state diagram
2. State table
3. State assignment
4. State-assigned table
5. Synthesize the circuit

We don't always need the state-assigned table, as the next state expressions can always be synthesized by inspection by looking at the arrows in the state diagram.

Using one FF/state is known as a **one-hot coding**

## FSMs in Verilog

Always 3 sections of code (state table, FFs, output)

```

module FSM(w, Clock, Resetn, z);
  input w, Clock, Resetn;
  output z;
  reg [2:1] y, Y;
  parameter A = 2'b00, B = 2'b01, C = 2'b10, D = 2'b11;

  // State table
  always @ (*)

```

```

case (y)
  A: if (w) Y = B; else Y = A;
  B: if (w) Y = B; else Y = C;
  C: if (w) Y = D; else Y = A;
  D: if (w) Y = B; else Y = C;
endcase

// State FFs
always @ (posedge Clock)
  if (!Resetn) y <= A;
  else y <= Y;

// FSM outputs
assign z = (y == D);
endmodule


```



### Regarding Case Statements

For some valuations, if we don't specify a default value, then the compiler may create unwanted latches

## Mealy FSMs

 

If the connection denoted by ☆ exists, then the outputs depend on both the present state  $y_1, \dots, y_k$  and the inputs. This is called a Mealy FSM. When the connection doesn't exist, it is called a Moore FSM.

### Example FSM Design (Arbiter)


- ?** Design an FSM that controls access to a shared resource, between three devices. Each device requests access to the resource by asserting a request signal  $r_1, r_2, r_3$ . The arbiter chooses which device gets the resource in each clock cycle by setting a grant output  $g_1, g_2, g_3$ . There is a priority scheme  $r_1 > r_2 > r_3$ .

## Memory Technology

Every computer system needs memory to hold data and programs. Also, other logic circuits might need to store some data.

In every memory there are two main parts:


1. Decoder
2. Array of storage cells

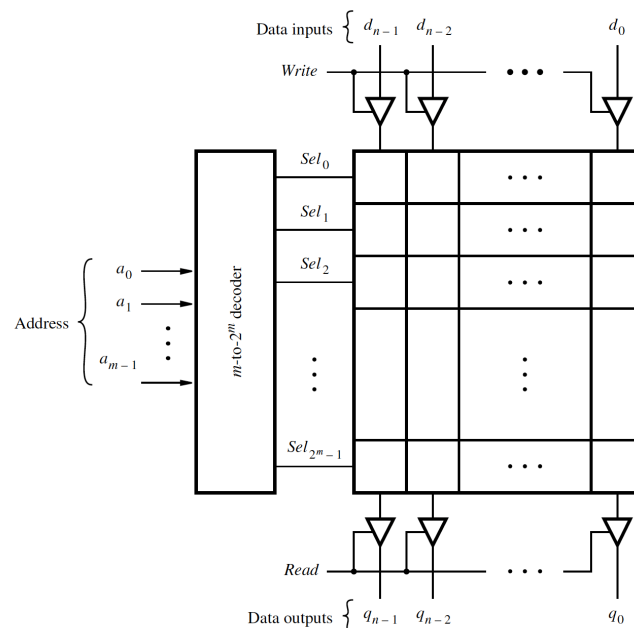

- The number of address inputs depends on the depth (number of words) of the memory
- The number of data input/output bits depends on the width (number of bits per word) of the memory
 
### Storage Cells

- Each storage cell in a memory holds one bit (0, or 1)



There are two main memory technologies:

1. Static

- a. Easy to use, but capacity is small due to "large" storage cell.
- b. Example: FPGA on chip memory in the DE1-SoC board is SRAM (static random access memory)

2. Dynamic


- a. Hard to use but capacity is large (due to "small" storage cell)
- b. Example: a computer using >1GB is always using DRAM

## FPGA On Chip Memory

The FPGA contains programmable logic blocks (for logic functions and FFs) but it also contains SRAM memory. Each block of memory has 10240 storage cells and 446 such blocks. These blocks can be figured to make memories of various aspect ratios (depth by width)

E.g. 19200 X 3 (VGA)

## Architecture Example for (32 X 4)

 

★ Data in/out are separate ports

★ These registers are always present

Reading:

1. Apply address of the desired word, and set  $we = 0$
2. wait for posedge clock
3. The desired word appears on DataOut

Writing:

1. Apply address, apply DataIn, set  $we = 1$
2. Wait for posedge clock
3. Write is complete


### On Chip Memory Variants

RAM — random access to memory

ROM — read-only memory



### Dual-Port RAM

 

### Signed Numbers (2's complement)


In general,  $-k = 2^n - k$

We can use 2's complement to partition the numbers with  $n$  bits into 1/2 positive and 1/2 negative



Shortcut: we can use  $((2^n - 1) - k) + 1$

 
We can use this shortcut to make an adder/subtractor  $A \pm B$



## The Shortest Cut


Keep all digits of  $k$  up to and including the first 1, then complement the rest

## Carry-Bypass Adder

 


★ The reg signal is 1 iff all four pairs of  $a_i, b_i$  are different. This is how we use the carry-bypass

 For larger adders, we can use multiple instances of this



 - What is the worst delay to get to  $c_8$ ?
  - Looking at adder 1, there are two cases:
    - If all pair of  $a_4b_4, \dots, a_7b_7$  are different, then  $c_8 = c_4$  (see the red note above)
    - Any pair of  $a_4b_4, \dots, a_7b_7$  are the same. In that case,  $c_8$  is independent of  $c_4$



## Verilog Code

```
module addn (Cin, A, B, Cout, S);
  parameter n = 4;
  input Cin;
  input [n-1:0] A, B;
  output reg Cout;
  output reg [n-1:0] S;
  reg [n:0] C;
  always @ (*) begin
    C[0] = Cin;
    for (integer k = 0; k < n; k = k + 1) begin
      S[k] = A[k]^B[k]^C[k];
      C[k+1] = (A[k] == B[k]) ? B[k] : C[k];
    end
  end
endmodule
```



```

    end
    Cout = C[k];
end
endmodule


```

- The statements in the for loop are simply repeated for each value of k. This only saves typing.


```
module addn (...);
    // port declarations
    parameter n = 4;
    always @ (*)
        {Cout, s} = A + B + Cin;
endmodule
```

## Multiplication (positives only)

[illegible]

 

## Timing Analysis

 

$t_{su}$  — FF setup time: This is a window of time before the active clock edge during which the D input of the flip flop should not change

$t_h$  — FF hold time: This is a window of time after the active clock edge for which the input D should remain unchanged

$t_{cQ}$  — FF clock to output delay: This is a propagation delay for a new value of  $Q$  to appear on after a clock edge

$$T_{min} = \frac{1}{F_{max}}$$

- In most examples we assume no clock skew, meaning that the clock signal arrives at all FFs at exactly the same time.

Moral of the story: Ensure that all FFs are connected directly to the same clock signal. Otherwise, we will be a bad engineer


What happens if  $t_{su}$  and/or  $t_h$  are violated?




For FFs, the ball on top of the hill represents metastability, where  $Q$  is neither 0 nor 1, after a clock edge that violates either timing parameter. After some random time period (but within that clock cycle),  $Q$  will randomly settle to either 0 or 1.

If  $Q_1$  becomes metastable, it will randomly settle to 0 or 1 before it gets stored into  $Q_2$ . Thus,  $Q_2$  is never metastable. This is called a synchronizer.

## Computer Hardware

 


 A processor consists of two parts: the datapath and the control.


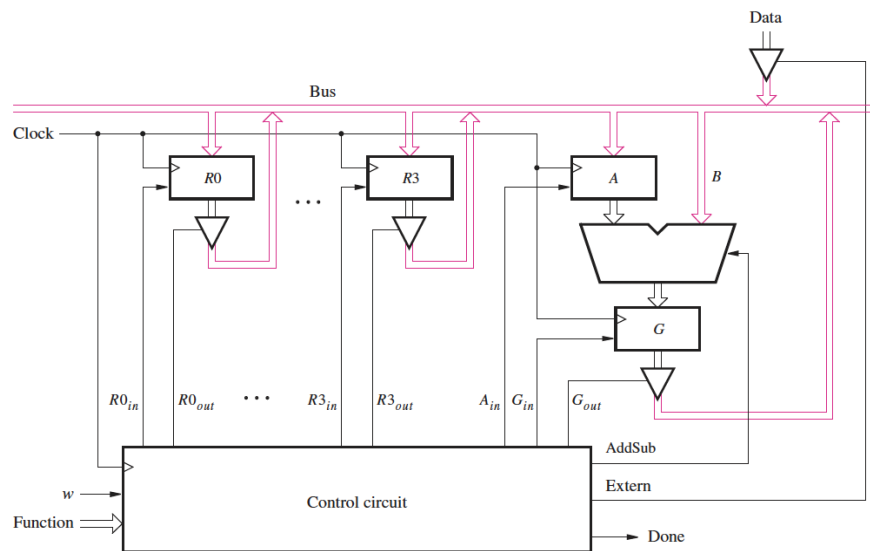
## Processor Design

Consider a set of  $n$ -bit registers  $R_0, \dots, R_7$ . We wish to initialize a registers contents, transfet reg→reg, add the contents of registers, and subtract.



We need to provide an instruction that tells the processor (FSM) what operation should be executed at any given time. We have to choose an encoding and decide what the instructions look like.

```
mv Rx,Ry // copy Rx←[Ry]
mvi Rx,#D // initialize Rx←D
add Rx,Ry // Rx←[Rx]+[Ry]
sub Rx,Ry // Rx←[Rx]-[Ry]
```

`mv` , `mvi` , `add` , `sub` are all called mnemonics

- We assume after reading the `mvi` instruction from DIN into IR, then the processor can next read #0 from DIN and use `set` to put it on the "bus."

- Some terminology:
  - `mv` , `mvi` , `add` , `sub` are called the assembly language instructions.
  - Every processor has a unique assembly language.
  - The **encoding** of instructions are called the opcodes
  - An Assembler program produces the opcodes and data which is called machine code
- Execution of instructions:
  - Each instruction appears on DIN, and is stored into IR. Call this clock cycle T0. Then, in the following clock cycle, the FSM will set the control signal as needed in each clock cycle to complete the instruction.

```

module proc (DIN, Resetn, Clock, Run, Done);
  input [7:0] DIN;
  input Resetn, Clock, Run;
  output reg Done;
  reg [2:1] T_D, t_Q;
  parameter T0 = 2'b00, T1 = 2'b01,...;
  parameter mv = 2'b00, mvi = 2'b01,...;
  ... other signals (yada-yada)
  // instantiate the components of the Dataport
  // FSM state table
  always @ (*)
    case (t_Q)
      T0: if (!Run) T_D = T0;
          else T_D = T1;
      T1: if (Done) T_D = T0;
          else T_D = T2;
      T2: T_D = T3;
      T3: T_D = T0;
    endcase
  // FSM outputs
  always @ (*) begin
    LR0 = 0; LR1 = 0;... LG = 0; Done = 0; LIR = 0;
    Sel = 3'bxx;

    case (y_Q)
      T0: LIR = 1;
      T1: case(II)
        mv: begin
          sel = YYY;
          LR = "XXX"; (*)
          Done = 1;
        end
    endcase
  end

```

```


endcase
endcase
end

```

(\*) = we would actually use a 3-8 decoder to produce LR0,...,LR7 from XXX.


- This processor needs to be enhanced to have an introduce to a memory. Instructions and data would come from that memory. Instructions and data would come from that memory
- We would add instructions to the processor for reading or writing memory.
- Finally, we need to be able to know where in the memory the instructions are stored. A special register which is a loadable counter, called a program counter (pc) is used for this.
  - Normally, pc is used as an address (transferred through ADDR to memory) from which to read the next instruction from memory.
  - The FSM always increments pc by 1 so it has the address of the next instruction.
  - Finally, pc can be loaded with any number (address) to implement loops.

## CMOS Technology

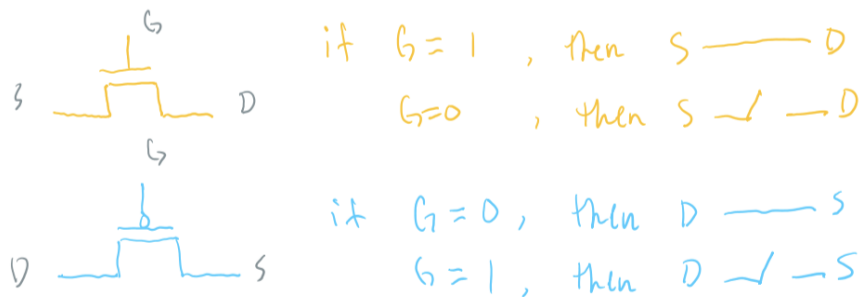

CMOS technology — complementary MOS

 - In CMOS, every circuit has an equal number NMOS and PMOS transistors.



- Without any voltage applied, these transistors are OFF, because of the charge under the gate being the opposite of the source/drain.
- In CMOS, there is never a path from  $V_{DD}$  to  $Gnd$  in the steady state. Thus, current flow is much smaller.
- 


### CMOS NAND Gate

$$f = \overline{x_1 x_2} = \overline{x_1} + \overline{x_2} \quad (\text{p-part})$$

for n-part

$$\overline{f} = \overline{\overline{x_1 x_2}} = x_1 x_2$$

$x_1$	$x_2$	$T_{p1}$	$T_{p2}$	$T_{N1}$	$T_{N2}$	$V_f$
0	0	ON	ON	OFF	OFF	1
0	1	ON	OFF	OFF	ON	1
1	0	OFF	ON	ON	OFF	1
1	1	OFF	OFF	ON	ON	0

 

### CMOS NOR Gate

$$f = \overline{x_1 + x_2} = \overline{x_1} \overline{x_2}$$

$$\overline{f} = \overline{\overline{x_1 + x_2}} = x_1 + x_2$$

$x_1$	$x_2$	$T_{p1}$	$T_{p2}$	$T_{N1}$	$T_{N2}$	$V_f$
0	0	ON	ON	OFF	OFF	1
0	1	ON	OFF	OFF	ON	0
1	0	OFF	ON	ON	OFF	0
1	1	OFF	OFF	ON	ON	0

