



# Textbook Notes

## MOSFET Amplifiers


### MOSFET Review + Non-Idealities

#### Body Effect


- in integrated circuits the substrate is shared across many MOS transistors
- to maintain the cutoff condition for all substrate-channel junctions, we connect the substrate to:
  - most negative power supply for NMOS
  - most positive power supply for PMOS
- resulting  $V_{SB}$  source-body voltage will be reverse-biased and affect device operation
- consider an NMOS whose substrate is negative relative to source then the depletion region will be widened and the channel depth will be reduced

$$V_t = V_{t0} + \gamma \left[ \sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f} \right]$$

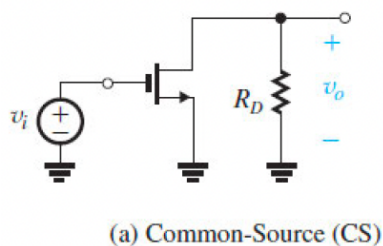
#### Basic MOSFET Amplifier Configurations



(a) Common-Source (CS)

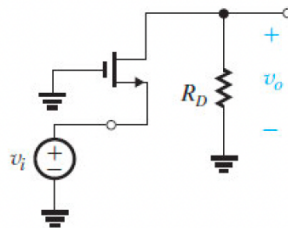


(b) Common-Gate (CG)

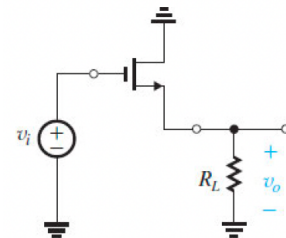

(c) Common-Drain (CD)  
or Source Follower
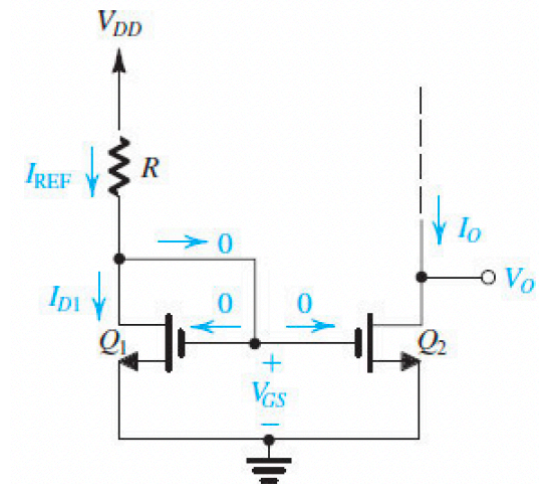
#### Current Mirrors

- current mirrors used to easily generate stable reference currents at various locations on the integrated circuit



- most basic relationship for the current mirror is:

$$\frac{I_O}{I_{REF}} = \frac{(W/L)_2}{(W/L)_1}$$

- $Q_2$  must be in saturation in order to supply a constant-current output, so we place a restriction on  $V_O$  such that

$$V_O \geq V_{OV}$$

- proper nomenclature:
  - PMOS current mirror is more aptly a current source
  - NMOS current mirror is more aptly a current sink

## Basic Gain Cell


- is a common-source amplifier driven by a bias current

$$\begin{aligned} R_{in} &= \infty \\ A_{vo} &= -g_m r_o \\ R_o &= r_o \end{aligned}$$

- the circuit has an intrinsic gain of  $g_m r_o$ , which with a little more manipulation we can find to be  $V_A/V_T$ , meaning it is entirely process dependent

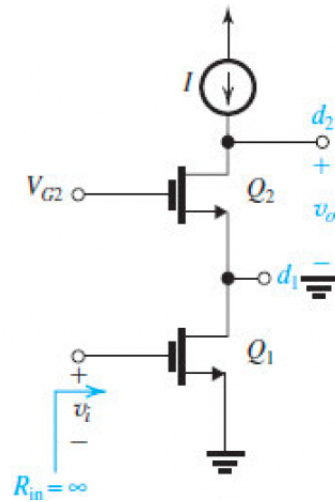
## Cascode Amplifiers

- cascoding is when we connect a common-gate transistor to provide current buffering in the output of a common-source amplifier
- current-buffering provides a higher output resistance, helps to increase the voltage gain



$$R_o = g_{m2}r_{o2}r_{o1}$$

### Cascode Current Mirror

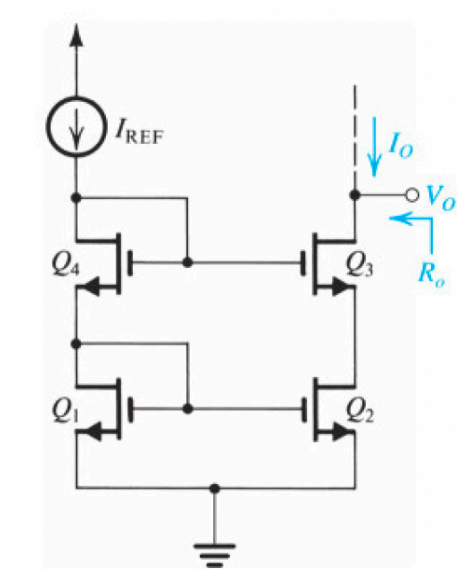


- for output resistance, we assume that because of low incremental resistances of the diode-connected transistors, the signal voltage at the gates of the bias voltages will be almost zero

$$R_o \approx g_{m3}r_{o3}r_{o2}$$

- cascoding increases output resistance of the current mirror by factor  $g_{m3}r_{o3}$
- drawback is that the cascode current mirror uses up a lot of available voltage
  - simple current mirror operates with  $V_{OV}$  across the output transistor, but
  - cascode current mirror requires a minimum voltage of  $V_t + 2V_{OV}$
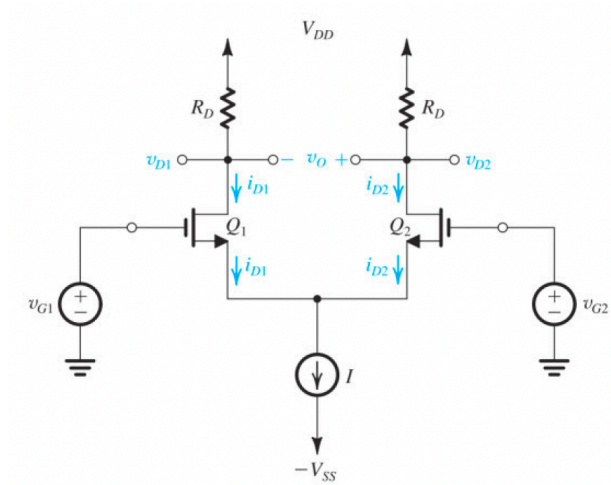
## Differential Amplifiers

- differential pair consists of two matched transistors whose sources are joined together and biased with a constant current source  $I$ 
  - current source is often itself a current mirror
  - for the time being let's assume the source is ideal with  $\infty$  output resistance



- we need two voltages to feed the differential pair

$$v_{G1} = V_{CM} + \frac{v_{id}}{2}$$

$$v_{G2} = V_{CM} - \frac{v_{id}}{2}$$

### Operation with Common-Mode Input

- when the two input voltages are the same (i.e., there is only a common-mode input voltage) then we see that the currents across the two transistors are the same as well

$$i_{D1} + i_{D2} = I$$

- the voltage at each of the drain terminals will be

$$V_{D1} = V_{D2} = V_{DD} - \frac{IR_D}{2}$$

- and the output voltage between the two drains will be 0, makes sense as there is no differential input applied and the currents through both transistors is the same
- another important aspect is the input common-mode range
  - highest value of  $V_{CM}$  is that  $Q_1$  and  $Q_2$  remain in saturation
  - lowest value of  $V_{CM}$  is that the current source must be allowed to produce current  $I$

$$V_{CM_{max}} = V_t + V_{D1,2} = V_t + V_{DD} - \frac{IR_D}{2}$$

$$V_{CM_{min}} = -V_{SS} + V_{OV_{mirror}} + V_t + V_{OV}$$


## Operation with Differential Input

- say we apply a differential input by grounding the gate of  $Q_2$  and applying a signal  $v_{id}$  to the gate of  $Q_1$ 
  - then we will have  $i_{D1} > i_{D2}$  and correspondingly  $v_{D1} < v_{D2}$
- for the bias current  $I$  to flow entirely in one of the two transistors (no sharing at all) then we need to first find value of  $v_{GS1}$

$$v_{GS1} = V_t + \sqrt{2}V_{OV}$$

- then we see that

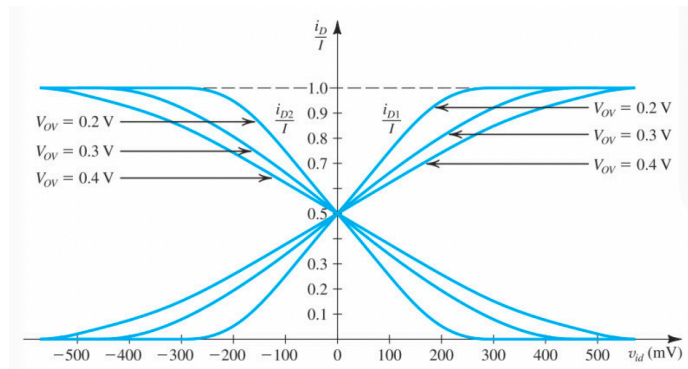
$$\begin{aligned} v_{id_{max}} &= v_{GS1} + v_S \\ &= V_t + \sqrt{2}V_{OV} - V_t \\ &= \sqrt{2}V_{OV} \end{aligned}$$



- the linear range of operation of the differential pair can be expanded by increasing the value of  $V_{OV}$  but then we also dissipate more power, which may be a serious limitation
- the difference in performance between a complementary/balanced input and a single-ended input is too subtle for us to care about right now
- when the output is taken between the two drains (as compared to one drain and ground) the signal will have a purely signal (no DC) component
- the signal voltage at the joint source connection must be zero, acting as a virtual ground
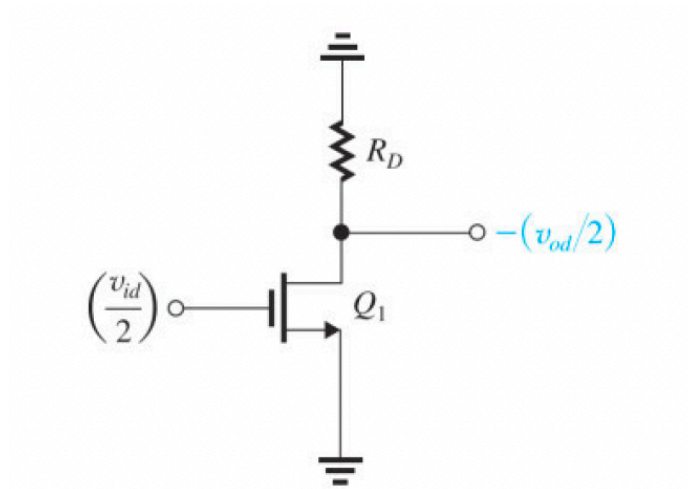
## The Differential Half-Circuit


- when a symmetrical differential amplifier is fed with a balanced differential input, then its performance can be determined by considering only a half-circuit



- then we see that the differential gain is given by

$$A_d = g_m(R_D || r_o)$$

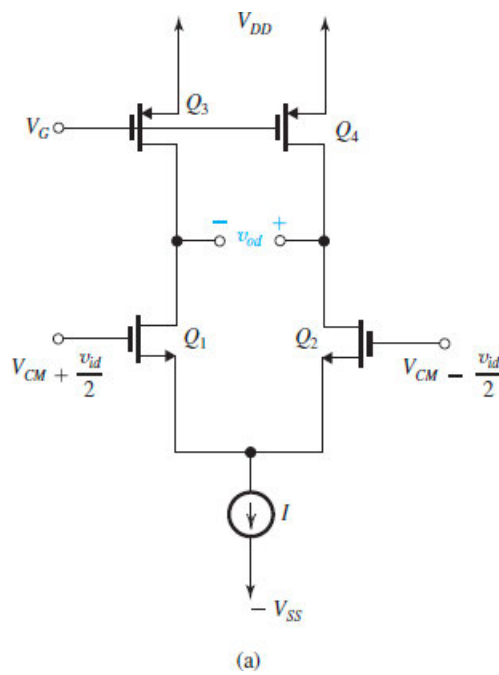
## Differential Amplifiers With Current-Source Loads



$$A_d = \frac{v_{od}}{v_{id}} = g_m(r_{o1} || r_{o3})$$
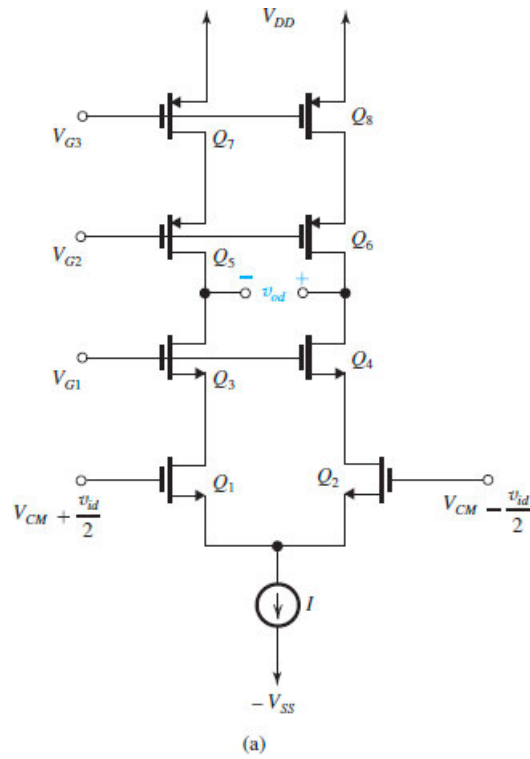
## The Cascode Differential Amplifier

- as we did with the current mirror, we can increase the gain of the differential amplifier using the cascode configuration



$$A_d = \frac{v_{od}}{v_{id}} = g_{m1}(R_{on} || R_{op})$$

$$R_{on} = (g_{m3}r_{o3})r_{o1}$$

$$R_{op} = (g_{m5}r_{o5})r_{o7}$$

## Power Amplifiers

Class A

Class B

Class AB

## Frequency Response